



<b>Course Name:</b>	<b>Hardware Description Language Lab (2UXL401)</b>	<b>Semester:</b>	<b>IV</b>
<b>Date of Performance:</b>	<b>27 / 04 / 2021</b>	<b>Batch No:</b>	<b>B2</b>
<b>Faculty Name:</b>	<b>Prof. Bhargavi Kaslikar</b>	<b>Roll No:</b>	<b>1912060</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	

**Experiment No: 7****Title:** FSM Implementation : Word Problem**Aim and Objective of the Experiment:**

Word problem for development of state diagram and design using VHDL.

To study FSM implementation in VHDL and to understand use of test bench for simulation.

**COs to be achieved:****CO 1:** Use basic Concurrent and Sequential statements in VHDL and write codes for simple applications**CO 2:** Test a VHDL code and verify the circuit model.**Work to be done**

Draw FSM for given problem. Upload VHDL codes for FSM developed from word problem. Also upload test bench and simulation for the same.

```
library ieee;
use ieee.std_logic_1164.all;

entity word_pro_naik is
    port(
        x: in std_logic_vector(1 downto 0);
        clk, rst : std_logic;
        y : out std_logic_vector(1 downto 0)
    );
end word_pro_naik;

architecture word_pro_naik_arch of word_pro_naik is
    type state is (reset, go_left, go_right, emergency);
    signal ps, ns : state := reset;

    begin
        process(clk, rst)
```

```

begin
  if(rst = '1')then
    ps <= reset;
    elsif(clk'event and clk = '1' )then
      ps <= ns;
    end if;
  end process;

  process(ps, x)
  begin
    if(x = "00") then
      ns <= reset;
    elsif (x = "01") then
      ns <= go_right;
    elsif (x = "10") then
      ns <= go_left;
    else
      ns <= emergency;
    end if;
  end process;

  process (ps) begin
    case ps is
      when reset => y <= "00";
      when go_left => y <= "10";
      when go_right => y <= "01";
      when emergency => y <= "11";
    end case;
  end process;
end word_pro_naik_arch;

library ieee;
use ieee.std_logic_1164.all;

entity word_pro_naik_tb is
end word_pro_naik_tb;

architecture word_pro_naik_tb_arch of word_pro_naik_tb is
  component word_pro_naik is
    port(
      x: in std_logic_vector(1 downto 0);
      clk, rst : std_logic;
      y : out std_logic_vector(1 downto 0)
    );
  end component;

```

```
signal x,y:std_logic_vector(1 downto 0);
signal rst:std_logic;
signal clk:std_logic:='0';
begin
  uut: word_pro_naik port map(x,clk,rst,y);
  clk<= not clk after 5ns;
```

```
process
begin
```

```
  rst <= '0';
  x<="00";
  wait for 10ns;
```

```
  x<="01";
  wait for 10ns;
```

```
  x<="10";
  wait for 10ns;
```

```
  x<="11";
  wait for 10ns;
```

```
  x<="01";
  wait for 10ns;
```

```
  x<="11";
  wait for 10ns;
```

```
  x<="10";
  wait for 10ns;
```

```
  x<="01";
  wait for 10ns;
```

```
  x<="00";
  wait for 10ns;
```

```
  x<="11";
  wait for 10ns;
```


```
  x<="10";
  wait for 10ns;
```

```
  x<="00";
```

wait for 10ns;

end process;

end word\_pro\_naik\_tb\_arch;

 


### Post Lab Subjective/Objective type Questions:

Upload Answer of following question before coming to next laboratory.

**Q1. Write a VHDL code for FSM implementation of a following state diagram.**

**Write a test bench for the same.**

 

Ans:

Main code:

library ieee;

use ieee.std\_logic\_1164.all;

entity postlab\_naik is

port(

clk,rst,i:in std\_logic;

y:out std\_logic

);

end postlab\_naik;

architecture postlab\_naik\_arch of postlab\_naik is

type mystate is (s0, s1, s2, s3, s4);

signal ps,ns:mystate:=s0;

begin

process(clk,rst)

begin

if(rst='1')then

ps<= s0;

elsif(clk'event and clk = '1' )then

ps<= ns;

end if;

```
end process;
```

```
process(ps,i) begin
```

```
    case ps is
```

```
        when s0 =>
```

```
            y <= '0';
```

```
            if(i = '0')then
```

```
                ns <= s0;
```

```
            else
```

```
                ns <= s1;
```

```
            end if;
```

```
        when s1 =>
```

```
            y <= '0';
```

```
            if(i = '0')then
```

```
                ns <= s2;
```

```
            else
```

```
                ns <= s1;
```

```
            end if;
```

```
        when s2 =>
```

```
            y <= '0';
```

```
            if(i = '0')then
```

```
                ns <= s3;
```

```
else

    ns <= s1;

end if;

when s3 =>

    y <= '0';

    if(i = '0')then

        ns <= s0;

    else

        ns <= s4;

    end if;

when s4 =>

    y <= '1';

    if(i = '0')then

        ns <= s0;

    else

        ns <= s1;

    end if;

end case;

end process;

end postlab_naik_arch;
```

TestBench:

```
library ieee;

use ieee.std_logic_1164.all;

entity postlab_naik_tb is
end postlab_naik_tb;

architecture postlab_naik_tb_arch of postlab_naik_tb is

component postlab_naik is
    port(
        clk,rst,i:in std_logic;
        y:out std_logic
    );
end component;

signal rst,i,y:std_logic;
signal clk:std_logic:='0';

begin

t1: postlab_naik port map(clk,rst,i,y);

    process begin
        clk <= '0';

        wait for 5ns;
```



```
        clk <= '1';

        wait for 5ns;

end process;

process

begin

    rst<= '0';

    i<='1';

    wait for 10ns;

    i<='0';

    wait for 10ns;

    i<='0';

    wait for 10ns;

    i<='1';

    wait for 10ns;

    i<='1';

    wait for 10ns;

    i<='1';

    wait for 10ns;

    i<='0';

    wait for 10ns;

    i<='0';

    wait for 10ns;

    i<='1';
```

wait for 10ns;

i<='0';

wait for 10ns;

i<='1';

wait for 10ns;


i<='0';

wait for 10ns;


end process;

end postlab\_naik\_tb\_arch;

State Machine:

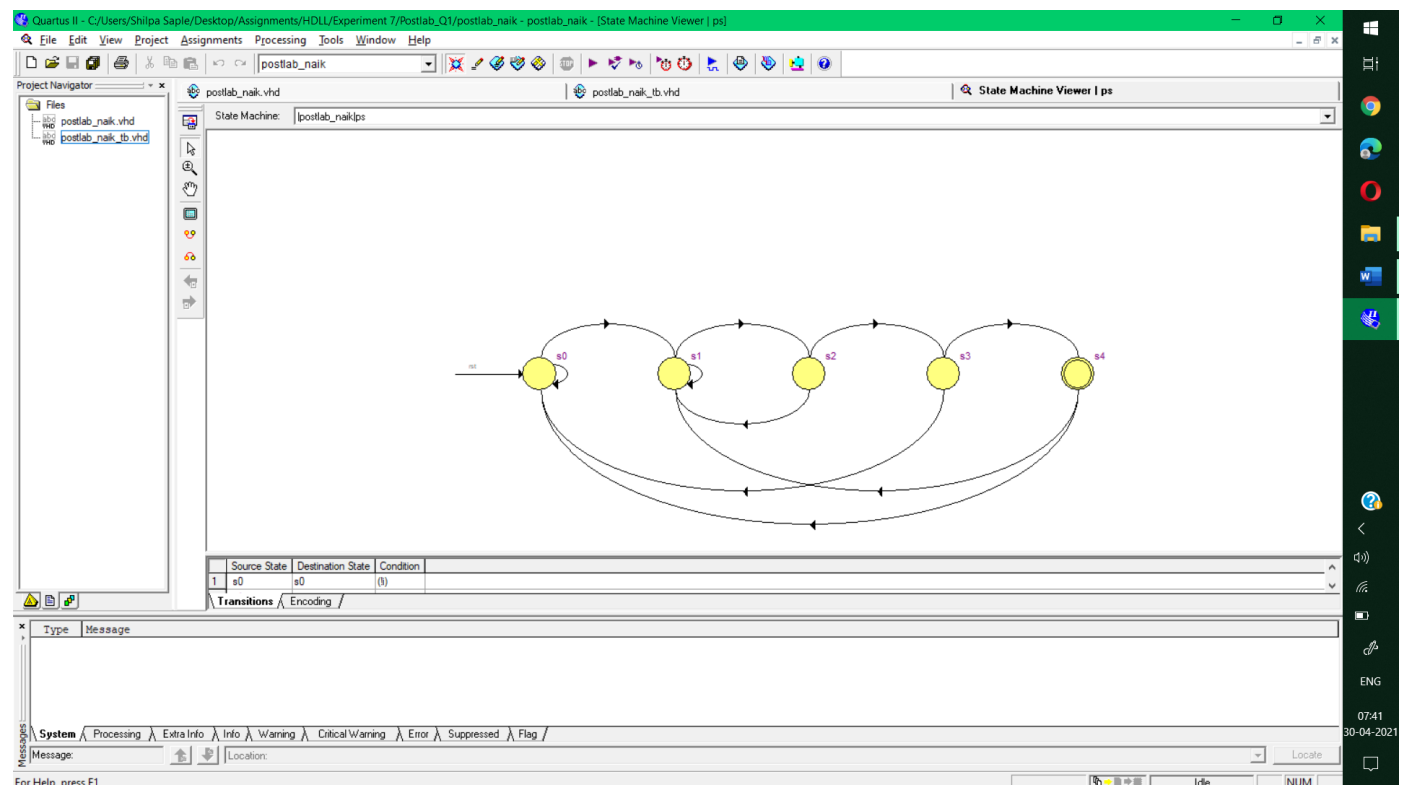

Output:

 

## Q2. Analyse the code and draw the state diagram

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity fsm is
    Port (
        ip1 : in std_logic;
        ip2 : in std_logic;
        ip3 : in std_logic;
        op1 : out std_logic;
        op2 : out std_logic;
        op3 : out std_logic;
        reset : in std_logic;
        clk : in std_logic
    );
```


```
end fsm;

architecture fsm_a of fsm is

    type state_t is (s_idle,s1,s2,s3);
    signal present_state, next_state : state_t;

    process(present_state,ip1,ip2,ip3)
    begin
        case present_state is
            when s_idle =>
                if (ip1 ='1') then
                    op1<='1'; op2<='0'; op3<='0';
                    next_state<= s1; elsif
                    (ip2='1') then
                        op1<='0'; op2<='1'; op3<='0';
                        next_state<= s2;
                    elsif (ip3='1') then
                        op1<='0'; op2<='0'; op3<='1';
                        next_state<= s1;
                    else
                        op1<='0'; op2<='0'; op3<='0';
                        next_state<= s_idle;
                    end if;
            when s1 =>
                if (ip1 ='1') then
                    op1<='1'; op2<='0'; op3<='0';
                    next_state<= s1;
                else
                    op1<='0'; op2<='0'; op3<='0';
                    next_state<= s_idle;
                end if;
            when s2 =>
                if (ip2 ='1') then
                    op1<='0'; op2<='1'; op3<='0';
                    next_state<= s2;
                else
                    op1<='0'; op2<='0'; op3<='0';
                    next_state<= s_idle;
                end if;
            when s3 =>
                if (ip3 ='1') then
                    op1<='0'; op2<='0'; op3<='1';
                    next_state<= s3;
                else
```
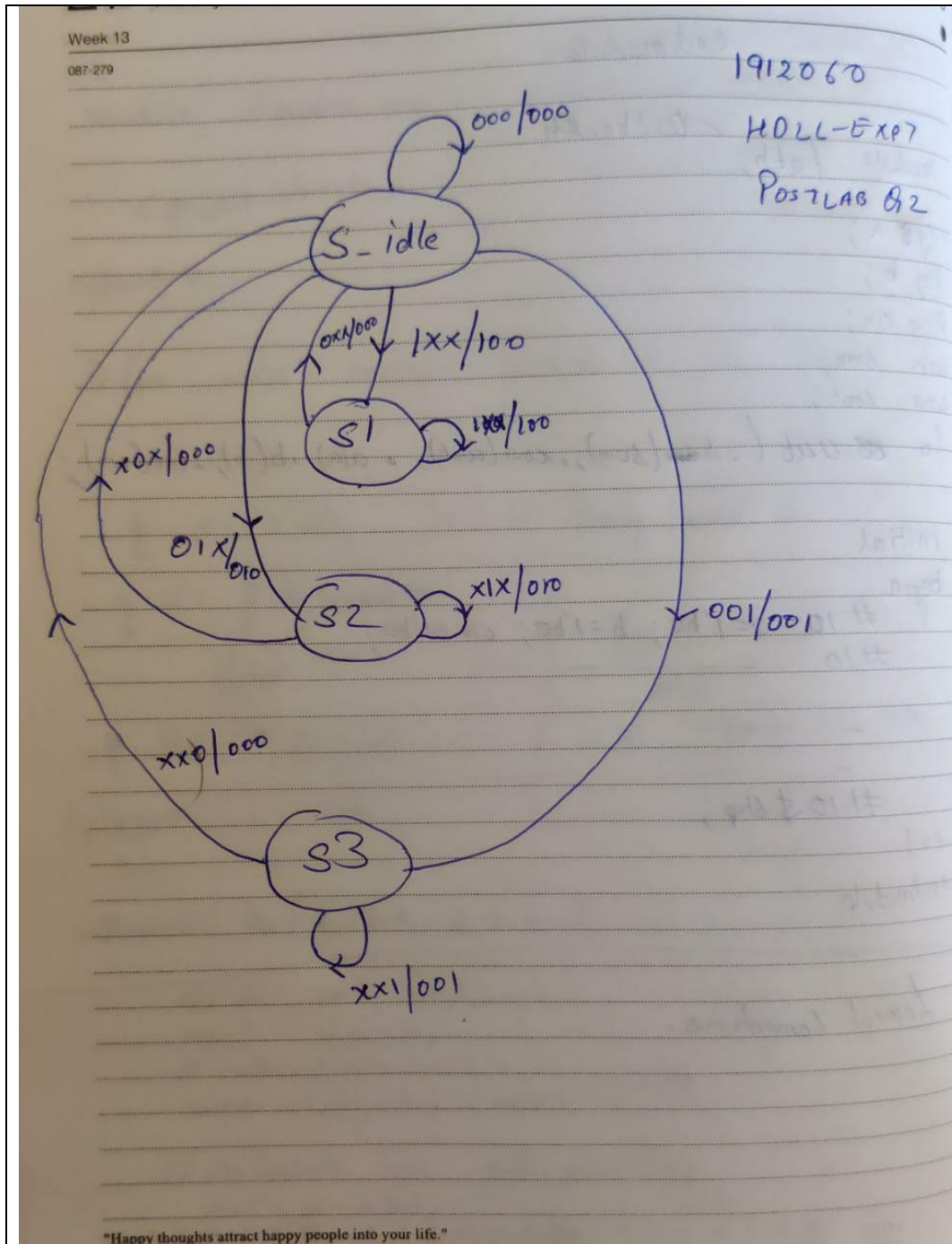
```
        op1<='0'; op2<='0'; op3<='0';
        next_state<= s_idle;
    end if;
end case;
end process;
process(clk,reset)
begin
    if reset = '1' then
        present_state <= s_idle;
    elsif clk'event and clk='1' then
        present_state<= next_state;
    end if; end
process; end
fsm_a;
```



### Conclusion:

Thus, in this experiment we have implemented a word problem (Vehicle Tail Light) by using finite state machine in VHDL.

**Signature of faculty in-charge with Date:**