

Course Name:	Hardware Description Language Lab (2UXL401)	Semester:	IV
Date of Performance:	07 / 04 / 2021	Batch No:	B2
Faculty Name:	Prof. Bhargavi Kaslikar	Roll No:	1912060
Faculty Sign & Date:		Grade/Marks:	

Experiment No: 5

Title: Use of sequential statements:

- Shift Registers using Flip flops
- Shift Registers using IC 74194

Aim and Objective of the Experiment:

- Write a VHDL code for implementing a 4-bit universal shift register with synchronous reset. It has 2 select inputs which control the operation as follows
00: pause
01: shift left
10: shift right
11: Rotate right
- Write a VHDL code to implement IC 74194
- Write a test bench to verify your results.
Also, generate a programming file and download the code on CPLD kit and verify the results.

Write a VHDL code

To study basic sequential statements of VHDL and to understand use of test bench for simulation.

COs to be achieved:

- CO 1:** Use basic Concurrent and Sequential statements in VHDL and write codes for simple applications
- CO 2:** Test a VHDL code and verify the circuit model.
- CO 3:** Synthesize and Implement the designed circuits on CPLD/ FPGA.

Work to be done

Upload VHDL codes for 4 bit universal shift register with synchronous reset. Also upload test bench and simulation for the same.

Upload scanned copy of post lab questions.

Shift Register Using JK FlipFlop:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity shift_reg_ff_naik is
port(
    rst,clk : in std_logic;
    output : out std_logic_vector(3 downto 0)
);
end shift_reg_ff_naik;

architecture shift_reg_ff_naik_arch of shift_reg_ff_naik is

    component jk_naik is
        port (
            JK: IN STD_LOGIC_VECTOR(1 downto 0);
            clock: IN STD_LOGIC;
            reset: IN STD_LOGIC;
            q: out STD_LOGIC
        );
    end component;

    signal temp_output:std_logic_vector(3 downto 0);
    signal temp1,temp2,temp3: std_logic_vector(1 downto 0);

begin
    FF1 : jk_naik port map("11" , clk , rst , temp_output(0));

    temp1 <= temp_output(0) & (not temp_output(0));
```

```
FF2 : jk_naik port map(temp1 , clk , rst , temp_output(1));
```

```
temp2 <= temp_output(1) & (not temp_output(1));
```

```
FF3 : jk_naik port map(temp2 , clk , rst , temp_output(2));
```

```
temp3 <= temp_output(2) & (not temp_output(2));
```

```
FF4 : jk_naik port map(temp3 , clk , rst , temp_output(3));
```

```
output <= temp_output;
```

```
end shift_reg_ff_naik_arch;
```

JK Flip Flop:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_arith.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
entity jk_naik is
```

```
    port (
```

```
        JK: IN STD_LOGIC_VECTOR(1 downto 0);
```

```
        clock: IN STD_LOGIC;
```

```
        reset: IN STD_LOGIC;
```

```
        q: out STD_LOGIC
```

```
    );
```

```
end jk_naik;
```

```
architecture jk_naik_arch of jk_naik is
```

```
    signal q_s : std_logic := '0';
```

```
    begin
```

```
        process(reset,clock)
```

```
        begin
```

```
            if (reset = '1')then
```

```
                q_s <='0';
```

```
            elsif (clock'event and clock = '1')then
```

```
                case (JK) is
```

```
                    when "00" => q_s <= q_s;
```

```
                    when "01" => q_s <= '0';
```

```
                    when "10" => q_s <= '1';
```

```
                    when others => q_s <= not q_s;
```


```
                end case;
```

```
        end if;  
    end process;  
    q <= q_s;  
end jk_naik_arch;
```


Shift Register using JK FlipFlop Testbench:

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
use ieee.std_logic_arith.all;  
  
entity shift_reg_ff_naik_tb is  
end entity;  
architecture shift_reg_ff_naik_tb_arch of shift_reg_ff_naik_tb is  
    component shift_reg_ff_naik is  
        port(  
            rst,clk : in std_logic;  
            output : out std_logic_vector(3 downto 0)  
        );  
    end component;  
    signal rst,clk : std_logic;  
    signal output : std_logic_vector(3 downto 0);  
    begin  
        SR : shift_reg_ff_naik port map(rst , clk , output);  
        process begin  
            clk <= '1';  
            wait for 10ns;  
            clk <= '0';  
            wait for 10ns;  
        end process;  
  
        process  
            begin  
                rst <= '0';  
                wait for 2000ns;  
                rst <= '1';  
                wait for 20ns;  
            end process;  
    end shift_reg_ff_naik_tb_arch;
```

RTL View:

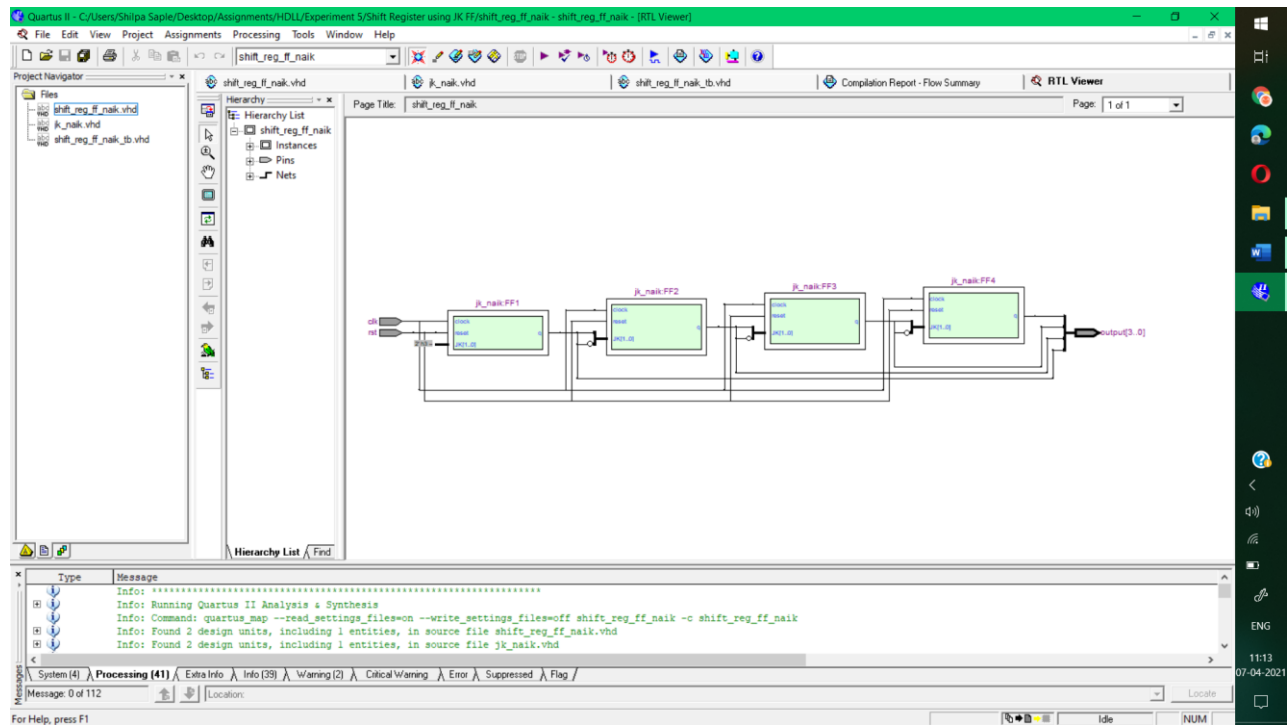

Output Waveform:

 

Shift Register

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity shift_register_naik is
  port ( clk, reset : in std_logic;
        select_inp : in std_logic_vector(1 downto 0);
        parallel_inp : in std_logic_vector(3 downto 0);
        output : out std_logic_vector(3 downto 0)
        );
end entity;

architecture shift_register_naik_arch of shift_register_naik is
  signal temp_output : std_logic_vector(3 downto 0);
begin
  process(clk,reset,select_inp,parallel_inp)
  begin
    if(reset='1') then
      temp_output <= "0000";
    elsif(clk'event and clk='1') then
      case select_inp is
        when "00" => temp_output <= temp_output;
        when "01" => temp_output <= temp_output(2 downto 0)&'1';
        when "10" => temp_output <= '1'&temp_output(3 downto 1);
        when "11" => temp_output <= parallel_inp;
        when others => temp_output <= "0000";
      end case;
    end if;
  end process;
  output <= temp_output;
end shift_register_naik_arch;
```

Shift Register Testbench:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity shift_register_naik_tb is
end entity;

architecture shift_register_naik_tb_arch of shift_register_naik_tb is
component shift_register_naik is
port ( clk, reset : in std_logic;
      select_inp : in std_logic_vector(1 downto 0);
      parallel_inp : in std_logic_vector(3 downto 0);
      output : out std_logic_vector(3 downto 0)
    );
end component;

signal clk,reset : std_logic;
signal select_inp : std_logic_vector(1 downto 0);
signal parallel_inp : std_logic_vector(3 downto 0);
signal output : std_logic_vector(3 downto 0);

begin
    SR : shift_register_naik port map(clk , reset , select_inp , parallel_inp , output);

    process
        begin
            clk <= '1';
            wait for 10ns;
            clk <= '0';
            wait for 10ns;
        end process;

        process
            begin
                reset <= '0';
                wait for 2000ns;
```

```
        reset <= '1';
        wait for 20ns;

    end process;

    process
        begin
            select_inp <= "11";
            parallel_inp <= "0110";
            wait for 20ns;

            select_inp <= "01";
            wait for 20ns;

            select_inp <= "10";
            wait for 30ns;


            select_inp <= "01";
            wait for 30ns;

            select_inp <= "10";
            wait for 20ns;


            select_inp <= "11";
            parallel_inp <= "1010";
            wait for 20ns;

        end process;
    end shift_register_naik_tb_arch;
```


RTL View:

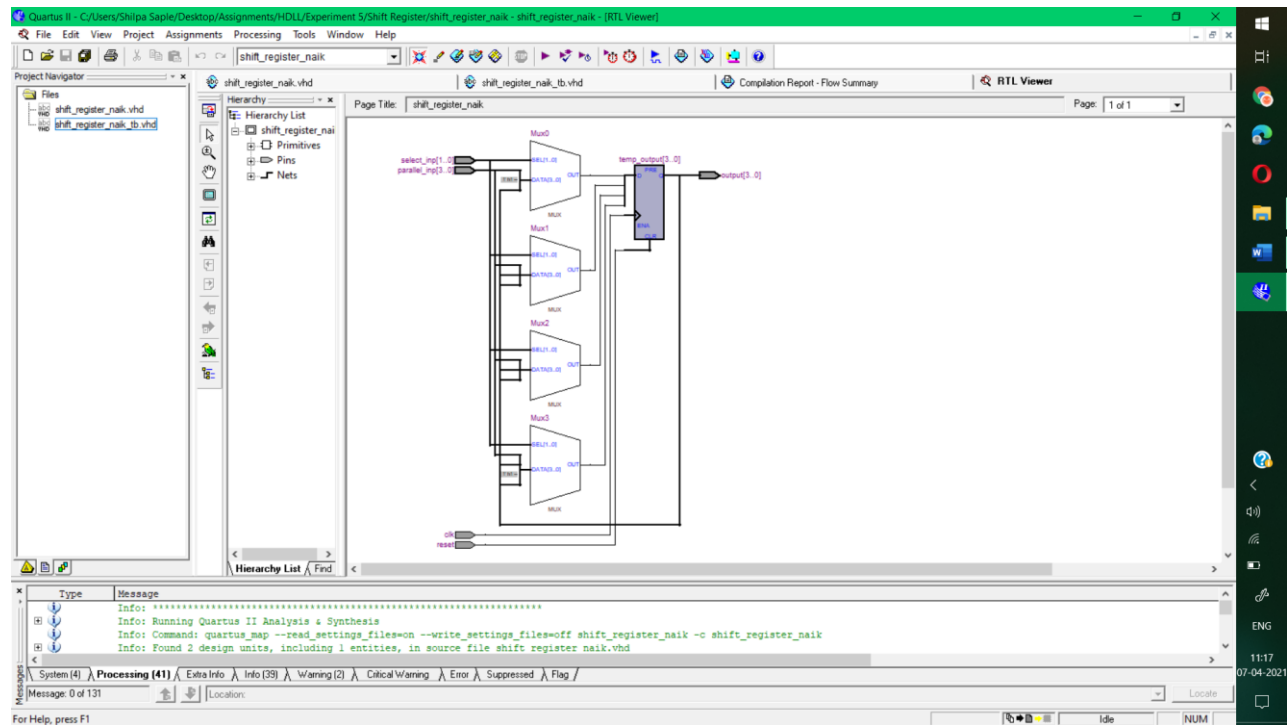

Output Waveform:

 

Post Lab Subjective/Objective type Questions:

Upload Answer of following question before coming to next laboratory.

Q1 Differentiate the properties of signal and variable. Give suitable example

NACHIKET NAIK - 1912060 - B2		HDL - Exp 5	
Q1) Signal		Variable	
<ul style="list-style-type: none"> Can be used inside/outside processes Can be used in multiple processes but can only be assigned in a single process Assigned using <code><=</code> Depend on if its a combinational / sequential code. It has a past history of values 		<ul style="list-style-type: none"> Can only be used inside processes Cannot be used in another process Assigned using <code>:=</code> Take the assigned value immediately Has a single current value. 	

Conclusion:

In this experiment we have used structural architecture to make a left shift register using flip flop and process, case statements to make a bidirectional shift register.

The shift register takes a select input which decides the mode of operation of the shift register.

For 00 - hold the current value

For 01 - left shift the current bits and add a '1' to the right

For 10 - right shift the current bits and add a '1' to the left

For 11 - the register accepts the parallel load input and loads the output with the parallel input

If reset input is given high then the output is reset to "0000".

To shift the bits we use the concatenation operator : &

Signature of faculty in-charge with Date: