

<b>Course Name:</b>	<b>Hardware Description Language Lab (2UXL401)</b>	<b>Semester:</b>	<b>IV</b>
<b>Date of Performance:</b>	<b>02/02/2021</b>	<b>Batch No:</b>	<b>B2</b>
<b>Faculty Name:</b>	<b>Prof. Bhargavi Kaslikar</b>	<b>Roll No:</b>	<b>1912060</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	

## Experiment No: 2


**Title:** Study of Multiplexer (Dataflow, Behavioral, Structural)

<b>Aim and Objective of the Experiment:</b>
<p>Write a VHDL code for implementing a 4:1 multiplexer</p> <ul style="list-style-type: none"> <li>a) Using when else construct ( Data Flow)</li> <li>b) Using structural architecture</li> </ul> <p>Write a testbench to verify your results.</p> <p>Write a VHDL code for 16: 1 mux using 4:1 mux and gates. ( Structural)</p> <p>To study basic types of architectures and to understand the use of concurrent statements.</p>


<b>COs to be achieved:</b>
<p><b>CO 1:</b> Use basic Concurrent and Sequential statements in VHDL and write codes for simple applications</p> <p><b>CO 2:</b> Test a VHDL code and verify the circuit model.</p> <p><b>CO 3:</b> Synthesize and Implement the designed circuits on CPLD/ FPGA.</p>

## Logic circuits:


### 4:1 Mux – Dataflow

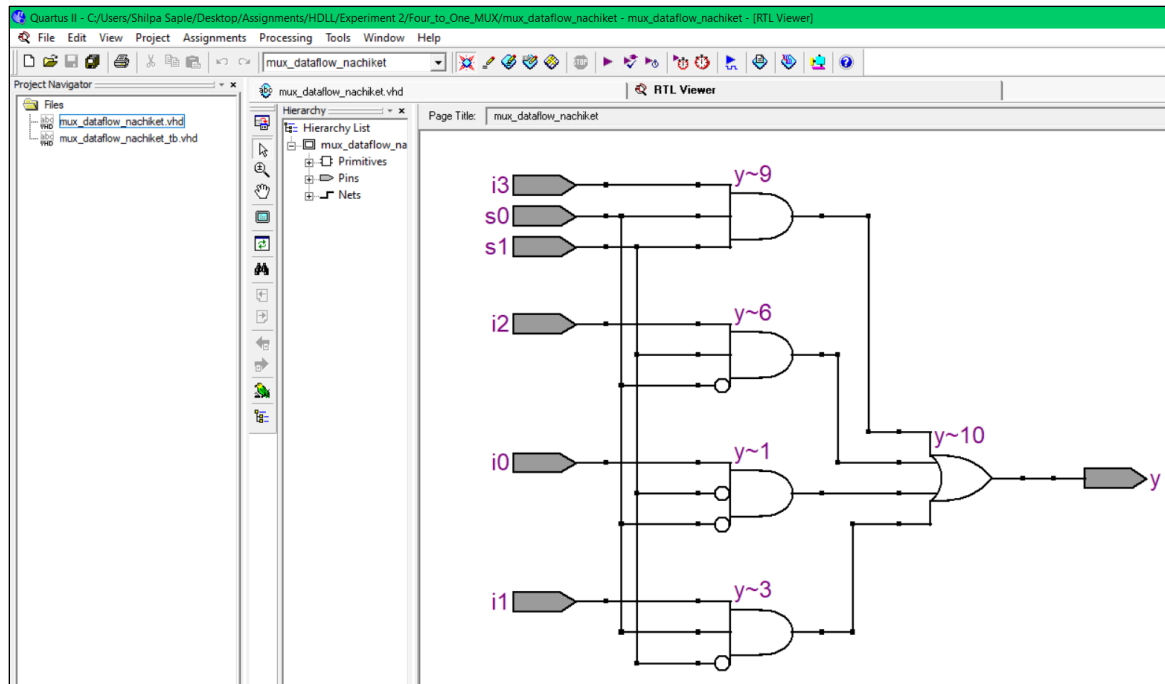


### 4:1 Mux – Structural

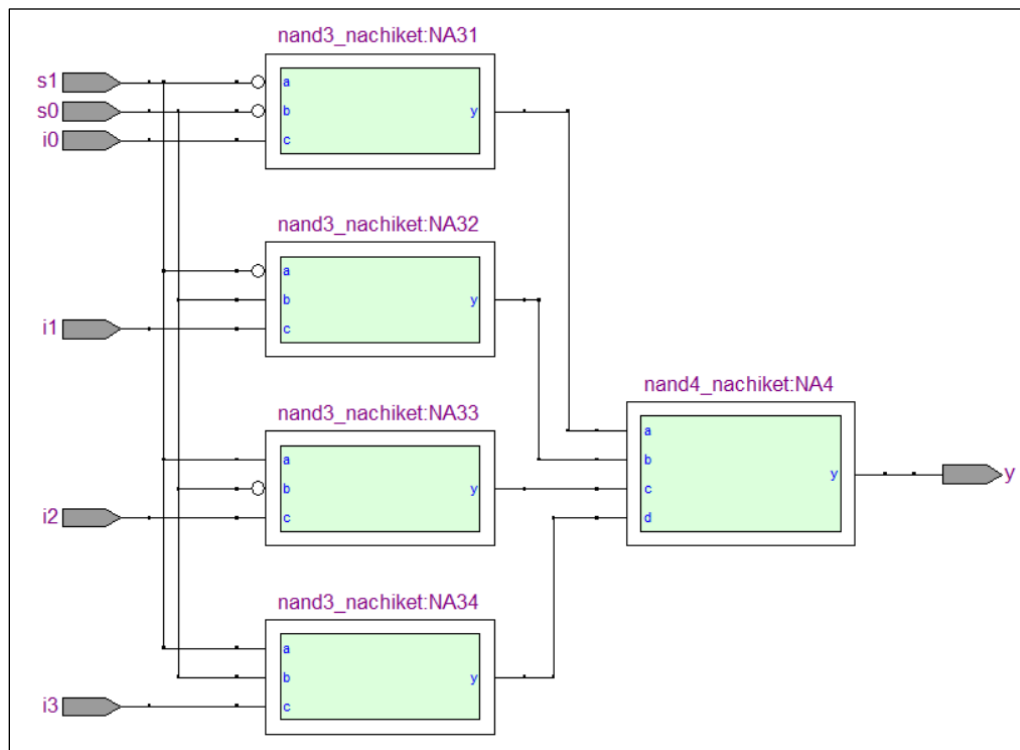

## 4:1 Mux – Behavioral

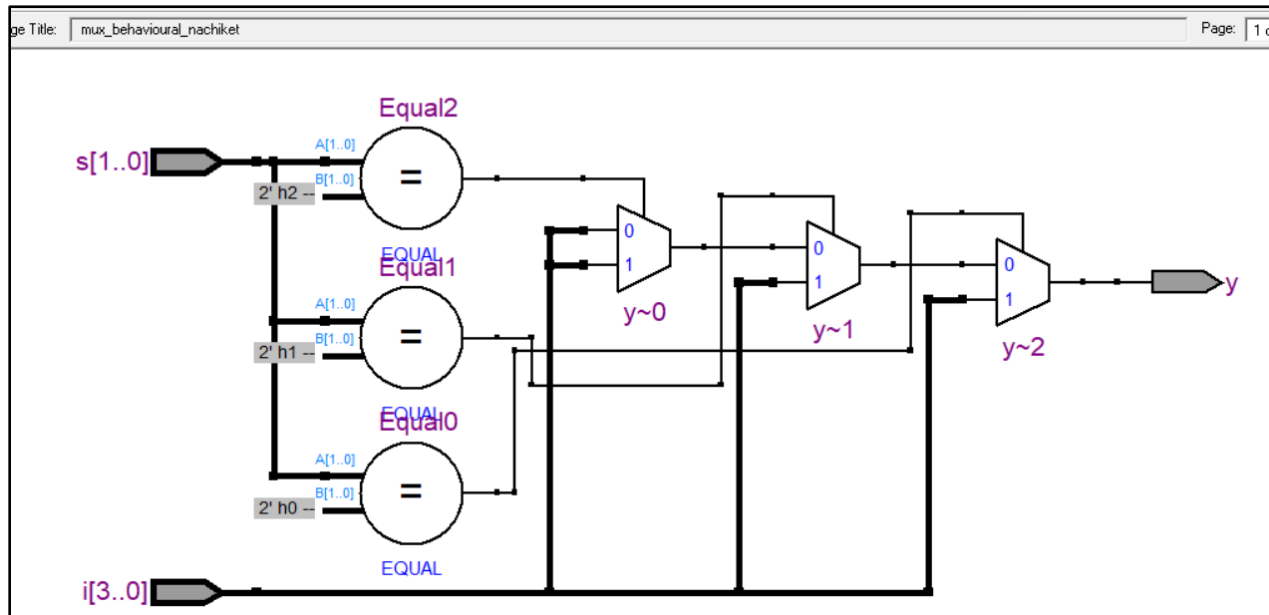

### 16:1 Mux – Structural

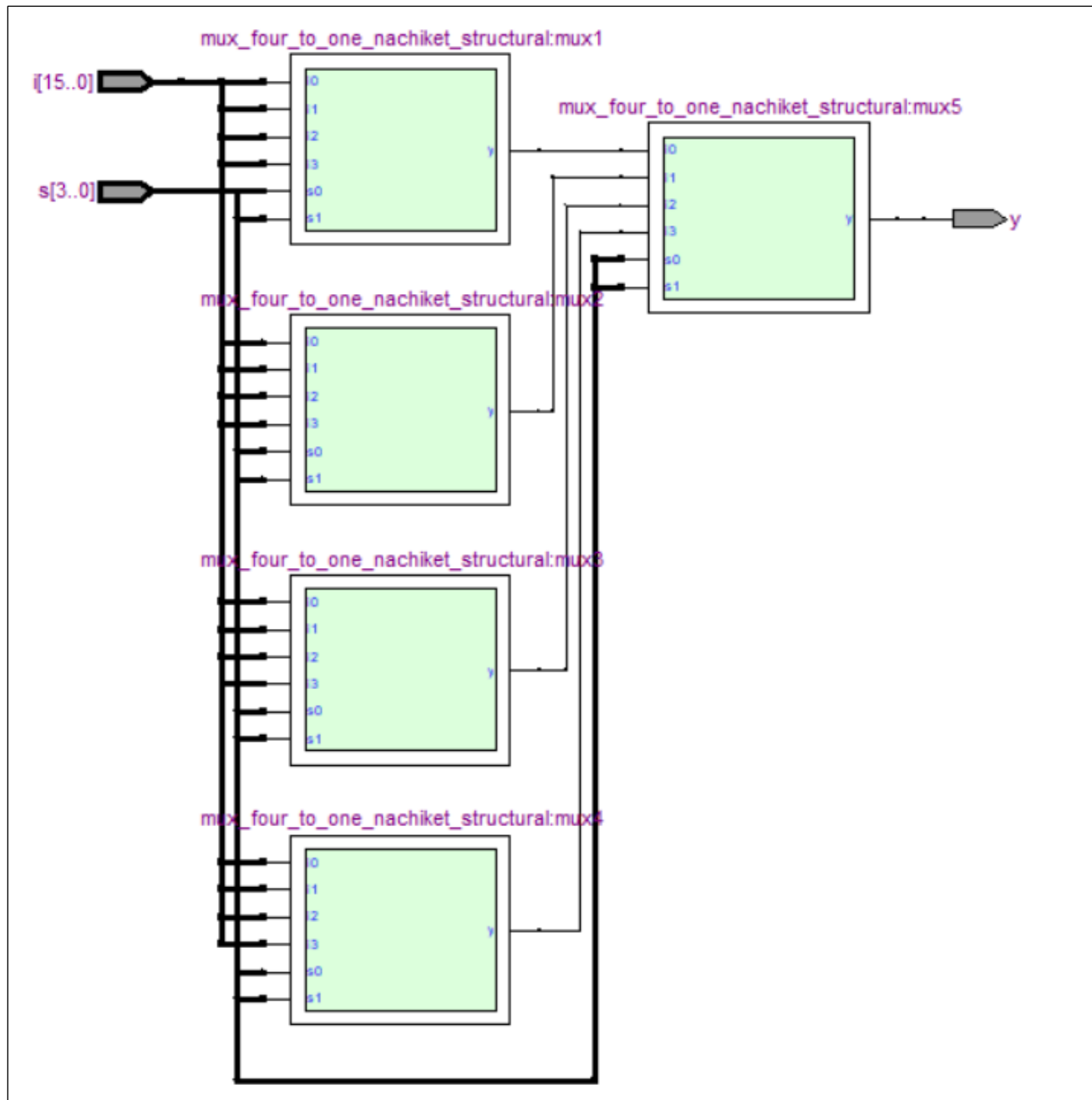

**Work to be uploaded**

Code for 4:1 Mux , Code for 16:1 mux

4:1 Data Flow:

library ieee;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_unsigned.all;

use ieee.std\_logic\_arith.all;

entity mux\_dataflow\_nachiket is

port(

i0,i1,i2,i3,s0,s1: In std\_logic;

y: Out std\_logic

);

end mux\_dataflow\_nachiket;

architecture mux\_dataflow\_nachiket\_arch of mux\_dataflow\_nachiket is

signal u1,u0:std\_logic;

begin

u1 <= not s1;

u0 <= not s0;

y<= (u1 and u0 and i0) or (u1 and s0 and i1) or (s1 and u0 and i2) or (s1 and s0 and i3) ;

end mux\_dataflow\_nachiket\_arch;

**4:1 Structural:**

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity mux_four_to_one_nachiket_structural is
    port(
        i0,i1,i2,i3,s0,s1: In std_logic;
        y: Out std_logic
    );
end mux_four_to_one_nachiket_structural;
architecture mux_four_to_one_nachiket_structural_arch of mux_four_to_one_nachiket_structural
is

    component nand3_nachiket is
        port(
            a,b,c: In std_logic;
            y: Out std_logic
        );
    end component;
    component nand4_nachiket is
        port(
            a,b,c,d: In std_logic;
            y: Out std_logic
        );
    end component;

    signal u1,u0,o0,o1,o2,o3:std_logic;
begin
    u1 <= not s1;
    u0 <= not s0;

    NA31: nand3_nachiket port map(u1,u0,i0,o0);
    NA32: nand3_nachiket port map(u1,s0,i1,o1);
    NA33: nand3_nachiket port map(s1,u0,i2,o2);
    NA34: nand3_nachiket port map(s1,s0,i3,o3);
    NA4: nand4_nachiket port map(o0,o1,o2,o3,y);
end mux_four_to_one_nachiket_structural_arch;
```

4:1 Behavioral:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity mux_behavioural_nachiket is
    port(
        i: In std_logic_vector(3 downto 0);
        s: In std_logic_vector(1 downto 0);
        y: Out std_logic
    );
end mux_behavioural_nachiket;

architecture mux_behavioural_nachiket_arch of mux_behavioural_nachiket is
    begin
        process(s,i)
            begin
                if(s="00") then
                    y <= i(0);
                elsif(s="01") then
                    y <= i(1);
                elsif(s="10") then
                    y <= i(2);
                else
                    y <= i(3);
                end if;
            end process;
        end mux_behavioural_nachiket_arch;
```

16:1 Mux using 4:1 Mux – Structural:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
use ieee.std_logic_arith.all;
```

```
entity mux_16_to_one_nachiket is
```

```
    port(
```

```
        i: In std_logic_vector(15 downto 0);
```

```
        s: In std_logic_vector(3 downto 0);
```

```
        y: Out std_logic
```

```
    );
```

```
end mux_16_to_one_nachiket;
```

```
architecture mux_16_to_one_nachiket_arch of mux_16_to_one_nachiket is
```

```
    component mux_four_to_one_nachiket_structural is
```

```
        port(
```

```
            i0,i1,i2,i3,s0,s1: In std_logic;
```

```
            y: Out std_logic
```

```
        );
```

```
    end component;
```

```
signal o: std_logic_vector(3 downto 0);
```

```
begin
```

```
    mux1: mux_four_to_one_nachiket_structural port map(i(0),i(1),i(2),i(3),s(0),s(1),o(0));
```

```
    mux2: mux_four_to_one_nachiket_structural port map(i(4),i(5),i(6),i(7),s(0),s(1),o(1));
```

```
    mux3: mux_four_to_one_nachiket_structural port map(i(8),i(9),i(10),i(11),s(0),s(1),o(2));
```

```
    mux4:                                mux_four_to_one_nachiket_structural                                port  
map(i(12),i(13),i(14),i(15),s(0),s(1),o(3));
```

```
    mux5: mux_four_to_one_nachiket_structural port map(o(0),o(1),o(2),o(3),s(2),s(3),y);
```

```
end mux_16_to_one_nachiket_arch;
```



Test bench for 4:1 mux and 16:1 Mux and simulation waveform of the same.

4:1 Testbench:

library ieee;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_unsigned.all;

use ieee.std\_logic\_arith.all;

entity mux\_dataflow\_nachiket\_tb is

end mux\_dataflow\_nachiket\_tb;

architecture mux\_dataflow\_nachiket\_tb\_arch of mux\_dataflow\_nachiket\_tb is

component mux\_dataflow\_nachiket is

port(

i0,i1,i2,i3,s0,s1: In std\_logic;

y: Out std\_logic

);

end component;

signal i0,i1,i2,i3,s0,s1,y: std\_logic;

begin

uut: mux\_dataflow\_nachiket port map( i0,i1,i2,i3,s0,s1,y);

process begin

i0<='1';

i1<='0';

i2<='1';

i3<='0';

s0<='0';

s1<='0';

wait for 20ns;

s0<='0';

s1<='1';

wait for 20ns;

s0<='1';

s1<='0';

```
wait for 20ns;
```

```
s0<='1';
```

```
s1<='1';
```

```
wait for 20ns;
```

```
end process;
```

```
end;
```

#### 4:1 Testbench Behavioral:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
use ieee.std_logic_arith.all;
```

```
entity mux_behavioural_nachiket_tb is
```

```
end mux_behavioural_nachiket_tb;
```

```
architecture mux_behavioural_nachiket_tb_arch of mux_behavioural_nachiket_tb is
```

```
    component mux_behavioural_nachiket is
```

```
        port(
```

```
            i: In std_logic_vector(3 downto 0);
```

```
            s: In std_logic_vector(1 downto 0);
```

```
            y: Out std_logic
```

```
        );
```

```
    end component;
```

```
    signal i: std_logic_vector(3 downto 0);
```

```
    signal s: std_logic_vector(1 downto 0);
```

```
    signal y: std_logic;
```

```
begin
```

```
    uut: mux_behavioural_nachiket port map(i,s,y);
```

```
    process begin
```

```
        i <= "1010";
```

```
        s <= "00";
```

```
        wait for 20ns;
```

```
s <= "01";
wait for 20ns;
```


```
s <= "10";
wait for 20ns;
```

```
s <= "11";
wait for 20ns;
```


```
end process;
```

end;

4:1 MUX waveform (dataflow):

 

#### 4:1 Waveform (Behavioral):

 

16:1 Testbench:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity mux_16_to_one_nachiket_tb is
end mux_16_to_one_nachiket_tb;

architecture mux_16_to_one_nachiket_tb_arch of mux_16_to_one_nachiket_tb is

    component mux_16_to_one_nachiket is
        port(
            i: In std_logic_vector(15 downto 0);
            s: In std_logic_vector(3 downto 0);
            y: Out std_logic
        );
    end component;
    signal i: std_logic_vector(15 downto 0);
    signal s: std_logic_vector(3 downto 0);
    signal y: std_logic;

    begin
        uut: mux_16_to_one_nachiket port map(i,s,y);

        process begin
            i <= "1011010010101011";

            s <= "0000";
            wait for 20ns;

            s <= "0001";
            wait for 20ns;
```

```
s <= "0010";  
wait for 20ns;
```

```
s <= "0011";  
wait for 20ns;
```

```
s <= "0101";  
wait for 20ns;
```

```
s <= "1010";  
wait for 20ns;
```

```
s <= "1101";  
wait for 20ns;
```


```
s <= "1110";  
wait for 20ns;
```

```
s <= "0110";  
wait for 20ns;
```

```
s <= "0111";  
wait for 20ns;
```

```
end process;  
end mux_16_to_one_nachiket_tb_arch;
```

## 16:1 Waveform:

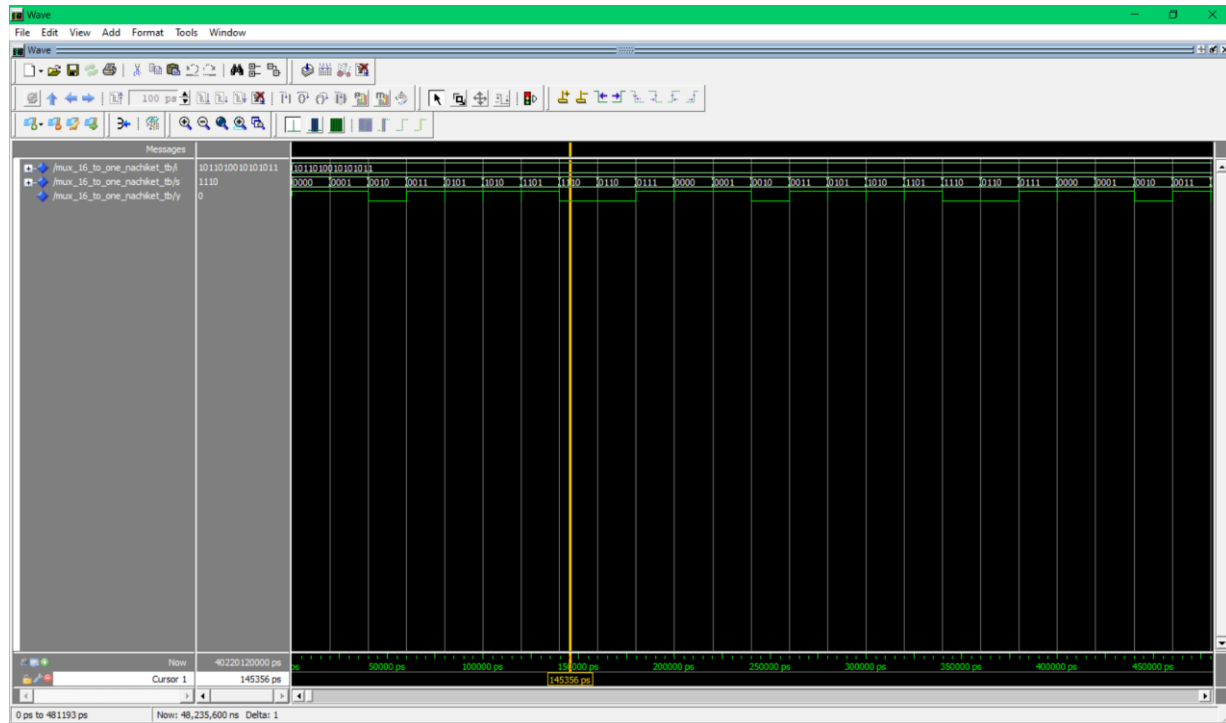

Scanned copy of post lab questions

**Post Lab Subjective/Objective type Questions:**

Upload Answer of following question before coming to next laboratory.

**Q1. Analyze the following code and explain its output.**

```
library ieee;
use ieee.std_logic_1164.all;

entity xyz is
    port(g1,g2,g3:in std_logic;
          sel: in std_logic_vector(2 downto 0);
          q:out std_logic_vector(7 downto 0)
    );
end xyz;

architecture xyz_a of xyz is
    signal q_s: std_logic_vector(7 downto 0);
Begin
    with sel select q_s<=
        "01111111" when "000",
        "10111111" when "001",
        "11011111" when "010",
        "11101111" when "011",
        "11110111" when "100",
        "11111011" when "101",
        "11111101" when "110",
        "11111110" when "111",
        "11111111" when others;
    q<=q_s when (g1 and not g2 and not g3)= '1'
    else "11111111";
end xyz_a_a;
```



Page No.:

Date:

YOUVA

NACHIKET NAIK - 1912060 - B2

HDL - EXP-2 - PostLAB

Q1)

~~Mistake~~ Error in the code:-

↳ Last line is given as `end xyz-a-a;`  
but it should be `end xyz-a;`

- The given entity `xyz` has 4 inputs, `g1`, `g2`, `g3` (std-logic i.e '0' or '1') and a `sel` (vector of 3 bits) and one output `q` of 8 bits.

- In the code we are also using a signal `q-s` which is a vector of 8 bits

- The value of `q-s` depends on that of `sel`.

- Whatever be the value of `sel`, that bit of `q-s` which is at the corresponding decimal value ~~index~~ of `sel` will be 0. Rest 7 bits will be 1.

Indexing starts from 0.

eg: if `sel = "101"` →  $(5)_{10}$  then the 6<sup>th</sup> bit of `q-s` will be 0 & others will be 1. ∴ `q-s = "1111011"`

This happens for `sel` in the range "000" to "111"

For any other value of `sel`, `q-s = "1111111"`

1912060

• Now, if the expression  $(g1 \text{ and not } g2 \text{ and not } g3)$   
= '1' then the output  $q = q-5$  else  $q$  will  
get the value "1111111"

• The expression is true only when  $g1 = 1, g2 = 0$   
 $g3 = 0$ .

**Q.2 Write a test bench for the above code.**

1912060

Q.2) Testbench :-

```
library ieee;
use ieee.std_logic-1164.all;
entity xyz_tb is
end xyz_tb;
architecture xyz_tb_arch of xyz_tb is
    component xyz is
        port (
            g1, g2, g3: in std_logic;
            sel: in std_logic_vector(2 downto 0);
            q: out std_logic_vector(7 downto 0);
        );
    end component;
```

```
signal g1, g2, g3: std_logic;
signal sel: std_logic_vector(2 downto 0);
signal q: std_logic_vector(7 downto 0);
```

```
begin
    uut: xyz port map (g1, g2, g3, sel, q);
    process begin
```

```
g1 <= '1';  
g2 <= '0';  
g3 <= '0';
```

```
sel <= "000";  
wait for 20 ns;
```

```
sel <= "001";  
wait for 20 ns;
```

```
sel <= "010";  
wait for 20 ns;
```

```
sel <= "011";  
wait for 20 ns;
```

```
sel <= "100";  
wait for 20 ns;
```

```
sel <= "101";  
wait for 20 ns;
```

```
sel <= "110";  
wait for 20 ns;
```

```
sel <= "111";  
wait for 20 ns;
```


```
g3 <= '1';  
sel <= "001";  
wait for 20 ns;
```

```

g3 <= '0';
g2 <= '1';
sel <= "010";
wait for 20 ns;
end process
end xyz - tb - arch;

```

Output of the above code:

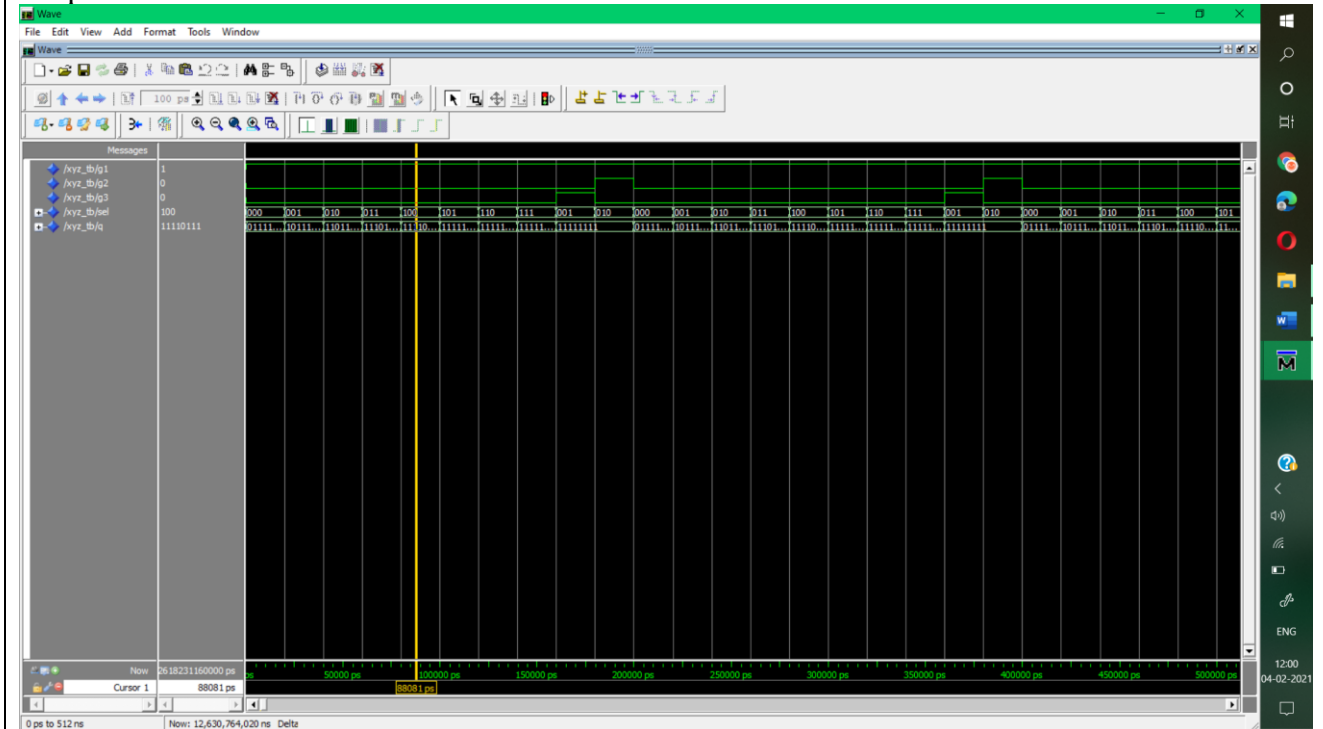



**Conclusion:**

NACHIKET NAIK - 1912060 - B2

HDL - EXP 2

CONCLUSION

↳ A multiplexer or MUX is a circuit that selects a single output from multiple inputs.

↳ In this experiment we wrote the code for 4:1 ~~to~~ by using both data flow and structural architecture.

↳ In dataflow, we specify the functionality of an entity by defining the flow of information.

↳ In structural architecture, the various components needed are declared first, then instances of components created with particular mappings of signal corresponds ~~the~~ to the various pins of components.

↳ Hence in dataflow of 4:1 mux, we used the SOP equation where as in structural, we created 2 more components: 3 input & 4 input NAND gates.

↳ Lastly, we implemented a 16:1 mux using 5, 4:1 mux (mux tree). Hence we used structural architecture as the circuit made use of predefined components.

**Signature of faculty in-charge with Date:**